




Lab 4

Part 1: SRAM Design

In your SRAM design, write 4'b1010 into the 32 address locations of the SRAM. After finishing writing, read data from RAM. Complete the design and run the test platform simulation in Verilog.

The SRAM is based on the following function table.

 WE	 CS	 OE	Function
X	L	X	High-z
L	H	L	High-z
L	H	H	Read Data
H	H	X	Write Data

Demo Requirement

You need to demonstrate the simulation waveform of the final top level design work to your lab instructor.

CPE166 Lab 4 Part 1

By: Prof. Pang

Note: Before starting this experiment, all the necessary knowledge required to complete this work has been introduced in the CPE166 lecture session. The following examples are for you to refresh your learning.

Sample Verilog Codes:

```

module ram ( address, data, cs, we, oe );
input  cs, we, oe ;
input [3:0] address ;
inout [7:0] data ;

reg [7:0] data_out ;
reg [7:0] mem [0:1023]; //10-bit address bus, 8-bit data bus.

assign data = (cs && oe && !we) ? data_out : 8'bzzzzzzzz;

always @ (cs or we or data or address)
if ( cs && we )
    mem[address] = data;

always @ (cs or we or data or address or data)
begin
    if (cs && !we && oe)
        data_out = mem[address];
end

endmodule

```

CPE166 Lab 4 Part 1

By: Prof. Pang

```

module mem_fsm ( clk, reset, address, data, cs, we, oe );
input          clk, reset;
output [3:0]   address;
inout [7:0]    data;
output         cs, we, oe;
reg           cs, we, oe;
reg [3:0]     address;
reg [7:0]     data_reg;
reg [2:0]     state;

parameter idle = 3'b000, s1= 3'b001, .... //decide the numeber of states you need to have
assign data = data_reg;

always@(posedge clk or posedge reset)
begin
    if (reset)
    begin
        state    <= idle;
        address <= 0;
    end
    else
    case (state)
        idle: begin
            state    <= s1;
            address <= 0;
        end

        s1:
            begin
                state <= s2;
            end
    endcase
end

```

CPE166 Lab 4 Part 1

By: Prof. Pang

```

        address <= 0;

    end

s2: begin

    address <= address + 1;

    if(address == 15)

        state <= s3;

    else

        state <= s2;

    end

....    // describe other states

default:

    begin

        state <= idle;

        address <= 0;

    end

endcase

end

always@(state)

begin

    case (state)

    idle: begin

        cs = 0;

        we = 0;

        oe = 0;

        data_reg = 8'bZZZZZZZZ;

    end

s1: begin    //writing

```

CPE166 Lab 4 Part 1

By: Prof. Pang

```
        cs = 1;

        we = 1;

        oe = 0;

        data_reg = 8'b11000011;
    end

s2: begin    //writing

        cs = 1;

        we = 1;

        oe = 0;

        data_reg = 8'b11000011;
    end

s3: begin    //reading

        cs = 1;

        we = 0;

        oe = 1;
    end

.... // determine other states

    default:

    begin

        cs = 0;

        we = 0;

        oe = 0;

        data_reg = 8'bzzzzzzzz;
    end

endcase

end

endmodule
```

CPE166 Lab 4 Part 1

By: Prof. Pang

More Instructions

Next, you need to develop top.v and create one instance of ram and another instance of mem_fsm to be able to write and read data using ram.

At last, create testbench to run simulations.

Your Project Design

Use the same approach described above to complete your project based on the project description.

Lab4. Simplified Microprocessor Design

The purpose of parts 2, 3, and part 4 of Lab 4 is to design a simplified microprocessor. Figure 4-1 shows a simplified microprocessor diagram having M0, M1, M2 and Cin inputs, one input SW1 and also clock input. The SW1 serves as asynchronous reset function.

Your design should finally implement the following operation:

$$R2 = M0 + (\text{not } M1) + \text{Cin}$$

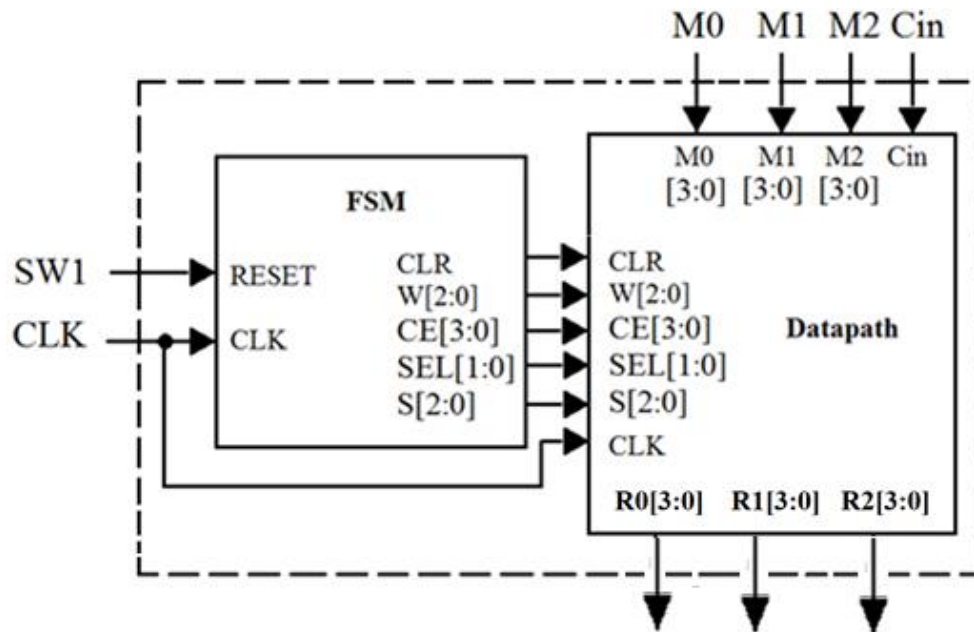


Figure 4-1. Simplified microprocessor block diagram

Part 2. Microprocessor Data Path Design

The detailed data path circuit is shown in Figure 4-2.

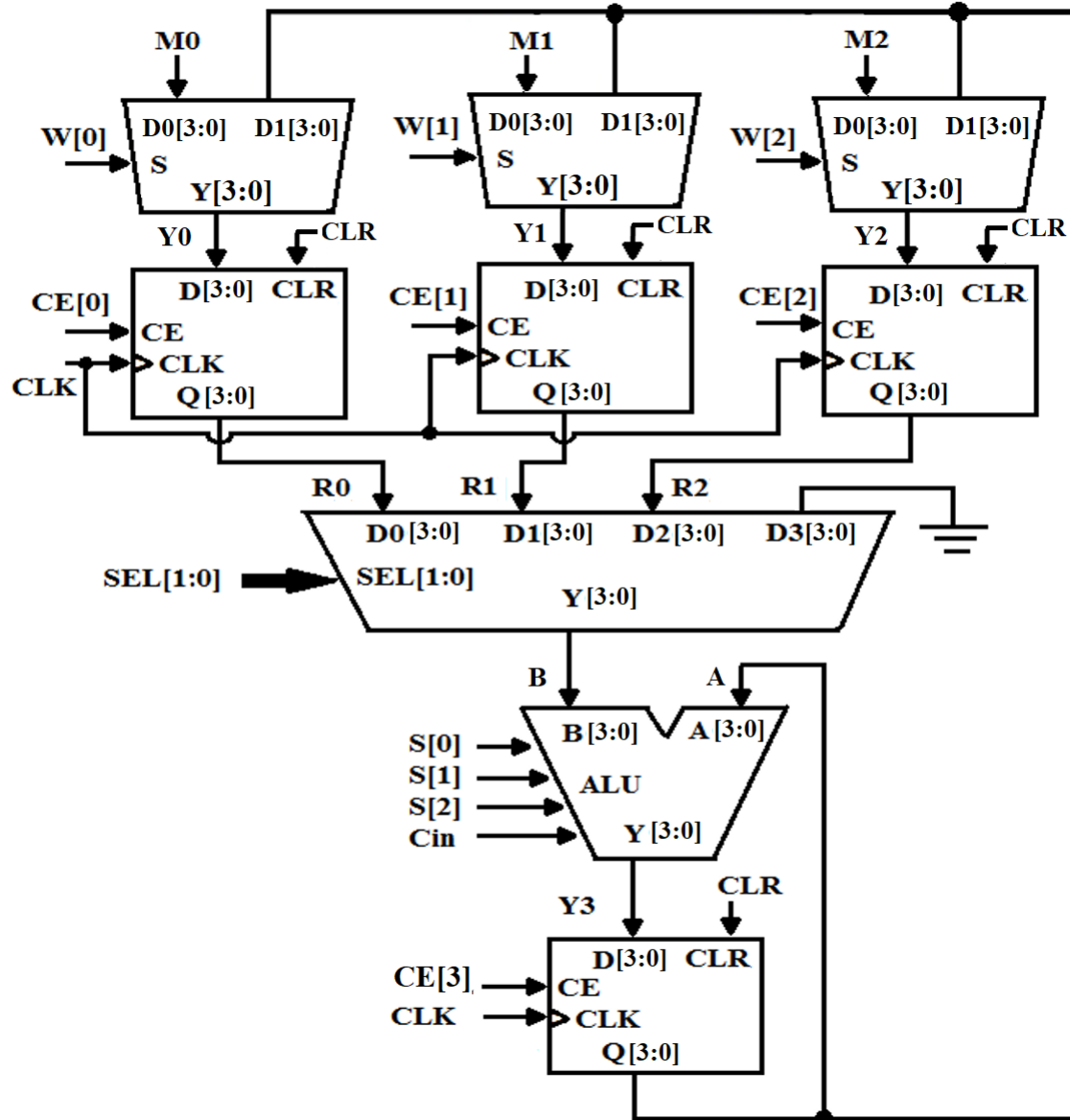


Figure 4-2. Simplified microprocessor data path circuit

The truth table of the ALU unit inside the data path circuit is shown in Table 4-1.

Table 4-1. ALU truth table

S[2]	S[1]	S[0]	ALU Output F
0	0	0	$F=A+B+C_{in}$
0	0	1	$F=A+B'+C_{in}$
0	1	0	$F=B$
0	1	1	$F=A$
1	0	0	$F=A \text{ AND } B$
1	0	1	$F=A \text{ OR } B$
1	1	0	$F=A'$
1	1	1	$F=A \text{ XOR } B$

Use structural hierarchical design method to implement the data path circuit. Design and simulate each individual sub-design. Wire each sub-design together to implement your final data path circuit.

For this simplified design, all inputs and outputs are only required to be 4 bits, carry output signal won't be used. For example, $A=(0110)_2$, $B=(1100)_2$, $C_{in}=1$, then $A+B+C_{in}=(0011)_2$.

Demo Requirement:

Show your testbench simulation of the top-level microprocessor data path design to your lab instructor.

Part 3. Microprocessor Control Path Design

Draw your finite state machine diagram for the “FSM” unit, which is used to implement the control path for the simplified microprocessor design shown in Figure 4-1. The control path block diagram is shown in Figure 4-3.

 


Figure 4-3. Simplified microprocessor control path block diagram

R0 and R1 are used to store operands M0 and M1 values.

R2 is used to store the final microprocessor operation result value, which is equal to:

$$M0 + (\text{not } M1) + \text{Cin}$$

Demo Requirement:

Show your testbench simulation of the microprocessor control path design to your lab instructor.

Part 4. Final 4-bit Microprocessor Design

This part is to complete the design shown in Figure 4-1 for the simplified 4-bit microprocessor.

Demo Requirement:

Demo your final simulation waveform of the top-level microprocessor design to your lab instructor.

Note, if you can demo part 4 successfully, you do not need to demo part 2, and part 3. After completing demo of part 4, you will get full credits of parts 2 ~ 4.

If you just demo part 2 or part 3 without completing part 4, you will be able to get credit for part 2 or part 3.